

CONTENTS

CHAPTER 1	1
WHAT MAKES GOOD SOUND?	1
CHAPTER 2	12
ENTHUSIAST v AUDIOPHILE	12
CHAPTER 3	29
ROOM ACOUSTICS	29
LISTENING ROOMS	32
ABSORBERS	33
DIFFUSERS	34
LIVE END v DEAD END	37
PRIORITIES IN TREATMENT	38
LOUDSPEAKER POSITIONING	40
SUB WOOFER	42
TIME DOMAIN ALIGNMENT	43
CHAPTER 4	46
TUBE SELECTIONS	46
VOLTAGE GAIN STAGES	48
DRIVER TUBES	51
POWER TUBES	54
TRANSMITTING TUBES	58
SPECIAL OLDIES	61
SMALL TRIODE CHARACTERISTICS	63
TUBE SELECTION PROCESS	65
RECTIFIER TUBES	86
DIRECTLY HEATED DIODES	90
INDIRECTLY HEATED DIODES	91
DAMPER DIODES	92
TUBE BASING	94
RECTIFIER TUBE BASING	98
DAMPER DIODE BASING	99
SPECIAL SOCKETS	100
CHAPTER 5	106
TRIODES	106
GENERALISED DESCRIPTION	107
DRIVE CLASS DEFINITIONS	109
TRIODE LOADINGS	111

SINGLE ENDED OPERATION	117
OPERATING SMALL TRIODES.....	122
CONSTANT CURRENT CIRCUITS	126
OPERATING POWER TRIODES	127
BIASING	131
GRID STOPPERS	133
GRID COMPONENTS	135
GRID CHOKES	137
PLATE COMPONENTS	140
LOUDSPEAKERS	148
CROSS OVERS	150
LOUDSPEAKER CABLES	154
CHAPTER 6	158
B+ POWER SUPPLIES	158
B+ UP TO 500 VOLTS (low power)	159
Solid state rectifying block	159
Single diode tube block	167
Capacitor assisted circuit	170
Cold tube arc over solution:	170
Reverse voltage flashover	172
Emission limitations	173
B+ ABOVE 500 VOLTS	175
Voltage doubler block	175
Soft Start Voltage Doubler	178
Totem Pole B+ Supply	179
Tube Diode bridge	180
Design notes	181
Ganging Solutions	185
D.C. to D.C. Convertors	186
CHOKES	187
SPECIAL PRECAUTIONS	188
CAPACITORS	191
STANDBY POWER SUPPLIES	198
HIGH VOLTAGE SWITCHING	200
Design notes	202
Technical details	204
CHAPTER 7	207
LOW VOLTAGE POWER	207
HEAVY CURRENT D.C. POWER SUPPLIES	207
FILAMENT SUPPLIES	211
FILAMENTARY TRIODES	232

CAPACITORS	249
CHAPTER 8	252
TRANSFORMERS	252
POWER TRANSFORMERS	253
Overview	253
Design Criteria	255
TRANSFORMER TYPES	256
EI Cores	256
Toroidal Cores	259
C Cores	259
R Cores	261
REGULATION	261
OUTPUT TRANSFORMERS	263
Grain Oriented silicon steel	264
Grain oriented silicon steel with interleaved nickel alloy laminations.	264
Permalloy comprising 80% silicon steel and 20% nickel	265
Cobalt Alloys	265
Pure Nickel	265
Ferrites	265
Amorphous cores	266
Mumetal	267
Design Notes	267
OPT Interleaving or Sectioning	268
Parafeed Transformers	269
INPUT TRANSFORMERS	270
CHOKES	272
Plate chokes	272
Power Chokes	273
Wideband chokes	274
Wire Considerations	275
CHAPTER 9	280
CHASSIS MATERIALS	280
COPPER CHASSIS	281
STAINLESS STEEL	282
WOOD CHASSIS	282
TEFLON CHASSIS	284
POLYCARBONATE	285
SILVER SHEET	286
ISOLATION TECHNIQUES	287
MOUNTING PRACTICES	288
FASTENERS	289

CHAPTER 10	291
GROUNDING PRACTICES	291
CHAPTER 11	308
TOPOLOGIES	308
Cascade Circuit	309
Mu Follower Circuit	311
SRPP Circuit	318
Cascode Circuit	320
Cathode Followers	323
Cathode Follower with Active Load	327
Cathode Follower using Fixed Bias	330
2A3 Interstage Circuit	332
Loftin White incl Shishido variation	336
Choke Loading	337
Parafeed	339
BIASING ARRANGEMENTS	342
Cathode Bypass	342
L.E.D. Bias	345
Battery Sourced Grid Bias	347
Battery sourced Cathode Bias	349
Psuedo Self Biasing	351
MOSFET CURRENT SOURCES	354
NON STANDARD CONFIGURATIONS	356
Totem Pole	356
211 Cathode driven pair	359
TRIAMPING SOLUTIONS	362
CHAPTER 12	365
SWITCHED MODE POWER SUPPLIES	365
PREAMBLE	366
SHORTCOMINGS	369
LIMITATIONS	370
TEST EQUIPMENT	371
TRANSFORMER CORE MATERIALS	372
CORE PROFILES	373
DIODES	376
FILTER CAPACITORS	377
WIRE	379
RESISTORS	382
DEVICES	383
DESIGN STRATEGY	385
CIRCUITS & SOLUTIONS	388

TRANSFORMER CONSTRUCTION	411
MODULE CONSTRUCTION	417
WORKING MODULES	420
WAVEFORMS	436
OUTPUT SNUBBERS	441
CHAPTER 13	456
REFERENCE MATERIALS	456
FORMULAE	459
GLOSSARY	460
INDEX	463
THE AUTHOR'S SYSTEM	474